

EE2230 Power electronics

Raktim Gautam Goswami (EE17BTECH11051)
Adarsh Bandi (CE17BTECH11010)

Group 36

September 24, 2019


Table of contents

- ① Problem statement
- ② Solution
- ③ Figure
- ④ Code

Problem statement

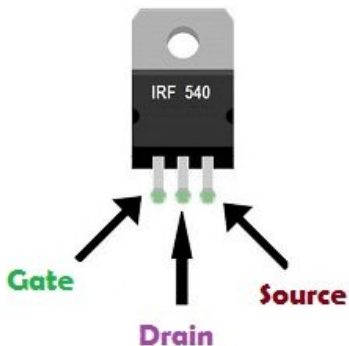Problem 4.1 Observe the output of the Source pin of the n-MOS on oscilloscope and write python script to generate the same.

Explanation: Below is the pinout diagram of n-MOS(IRF 540)



Explanation contd.

We connect the source pin of n-MOS with the pin5 of TLP350(according to the connections mentioned in manual).

TLP350 is a power amplifier that accepts low power input and produces high current input to the n-MOS(IRF 540)

The output shown on the oscilloscope is of a square wave pulse with amplitude of 10 and time period of 0.2 msec.

Figure

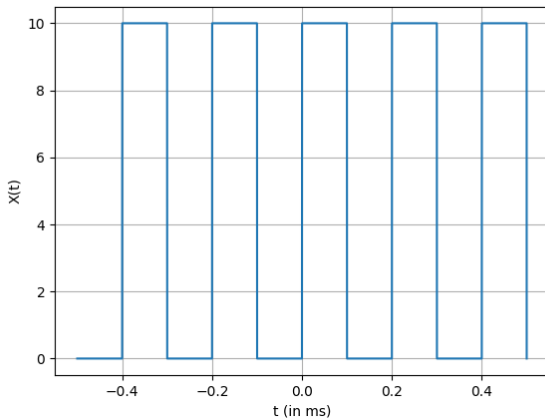


Figure: Output of the source pin

<https://github.com/rakimgg/Power-Electronics/blob/master/Presentation1/p1.py>